

$A \leq K H \leq 2$ $K \leq 1$ $A \leq$

1

$$f = ;$$
$$T = 0,001s$$

$$f = \frac{1}{T} \Rightarrow f = \frac{1}{0,001} = \frac{1}{1 \cdot 10^{-3}} =$$

$$f = 10^3 \text{ Hz} \Rightarrow \boxed{f = 1000 \text{ Hz}}$$

2.

$$f_1, T_1$$
$$f_2 = 2f_1$$
$$T_2 = ;$$

$$\left. \begin{array}{l} f_1 = \frac{1}{T_1} \\ f_2 = \frac{1}{T_2} \end{array} \right\} \begin{array}{l} f_1 = \frac{1}{T_1} \\ 2f_1 = \frac{1}{T_2} \end{array} \Rightarrow \frac{\cancel{f_1}}{2\cancel{f_1}} = \frac{\frac{1}{T_1}}{\frac{1}{T_2}} \Rightarrow$$

$$\Rightarrow \frac{1}{2} = \frac{T_2}{T_1} \Rightarrow 2T_2 = T_1 \Rightarrow$$

$$\Rightarrow \boxed{T_2 = \frac{T_1}{2}}$$

3

$$U_m = ;$$
$$U_{\text{eff}} = 220V$$

$$U_{\text{eff}} = \frac{U_m}{\sqrt{2}} \Rightarrow U_m = U_{\text{eff}} \cdot \sqrt{2} \Rightarrow$$

$$U_m = 220V \cdot 1,413 \Rightarrow$$

$$U_m = 220V \cdot 1,413 \Rightarrow$$

$$\boxed{U_m = 311V}$$

4

$$U = 220V$$

$$I = 15A$$

$$a) \cos \phi = 0,8$$

$$P = ;$$

$$b) Z = ;$$

a)

$$P = U \cdot I \cdot \cos \phi \Rightarrow$$

$$P = U \cdot I \cdot \cos \phi = 220V \cdot 15A \cdot 0,8 \Rightarrow$$

$$P = 3300 \cdot 0,8 \Rightarrow \boxed{P = 2640W}$$

b)

$$I = \frac{U}{Z} \Rightarrow Z = \frac{U}{I} = \frac{220V}{15A}$$

$$\Rightarrow \boxed{Z = 14,67\Omega}$$

5

$$U = 220V$$

$$I = 3A$$

$$P = 502W$$

$$\cos \phi = ;$$

$$P = U \cdot I \cdot \cos \phi \Rightarrow \cos \phi = \frac{P}{U \cdot I} =$$

$$\cos \phi = \frac{502}{220 \cdot 3} \Rightarrow \cos \phi = \frac{502}{660} \Rightarrow$$

$$\boxed{\cos \phi = 0,76}$$

6

$$X_C = ;$$

$$C = 0,2 \mu F = 0,2 \cdot 10^{-6} F$$

$$a) f_1 = 1 kHz = 1 \cdot 10^3 Hz$$

$$b) f_2 = 10 kHz = 10 \cdot 10^3 Hz$$

a)

$$X_{C1} = \frac{1}{2\pi f_1 \cdot C} \Rightarrow X_{C1} = \frac{1}{2 \cdot 3,14 \cdot 1 \cdot 10^3}$$

$$\Rightarrow X_{C1} = \frac{1}{2 \cdot 3,14 \cdot 1 \cdot 10^3 \cdot 0,2 \cdot 10^{-6}}$$

$$\Rightarrow X_{C1} = \frac{1}{6,28 \cdot 10^{-3} \cdot 0,2} \Rightarrow$$

$$\Rightarrow X_{C1} = \frac{10^3}{1,256} \Rightarrow \boxed{X_{C1} = 796\Omega}$$

$$b) X_{C2} = \frac{1}{2\pi f_2 \cdot C} \Rightarrow X_{C2} = \frac{1}{2 \cdot 3,14 \cdot 10 \cdot 10^3 \cdot 0,2 \cdot 10^{-6}}$$

$$\Rightarrow X_{C2} = \frac{1}{6,28 \cdot 10^{-2} \cdot 0,2} \Rightarrow X_{C2} = \frac{10^2}{1,256} \Rightarrow$$

$$\Rightarrow \boxed{X_{C2} = 79,6 \Omega}$$

7.

$$U = 220V$$

$$f = 50Hz$$

$$I = 0,1 A$$

$$(P = 0)$$

$$a) X_C = ;$$

$$b) C = ;$$

$$a) X_C = \frac{U}{I} \Rightarrow X_C = \frac{220V}{0,1A} \Rightarrow$$

$$\boxed{X_C = 2200 \Omega}$$

$$b) X_C = \frac{1}{2\pi f \cdot C} \Rightarrow C = \frac{1}{2\pi f \cdot X_C}$$

$$\Rightarrow C = \frac{1}{2 \cdot 3,14 \cdot 50 \cdot 2200} \Rightarrow$$

$$\Rightarrow C = \frac{1}{314 \cdot 2200} \Rightarrow$$

$$\Rightarrow C = \frac{1}{690800} \Rightarrow \boxed{C = 1,447 \cdot 10^{-6} F}$$

m

$$C = 1,447 \mu F$$